

Contributor Name-Sumanto Kar

Institute-Fr. Conceicao Rodrigues College of Engineering, Bandra

Year-2020

Title of the experiment

BJT based Differential Amplifier

Theory:

The electronic amplifier used for amplifying the difference between two input signals can be called as a differential amplifier. In general, these differential amplifiers consist of two terminals namely inverting terminal and non-inverting terminal. These inverting and non-inverting terminals are represented with – and + respectively.

The differential amplifier can be considered as an analog circuit which consists of two inputs and one output.

The output voltage of a differential amplifier is proportional to the difference between the two input voltages. This can be represented in equation form as follows:

$$V_{out} = A(V_{in}^+ - V_{in}^-)$$

Schematic diagram:

The circuit schematic of the BJT based Differential Amplifier in eSim is as shown below:

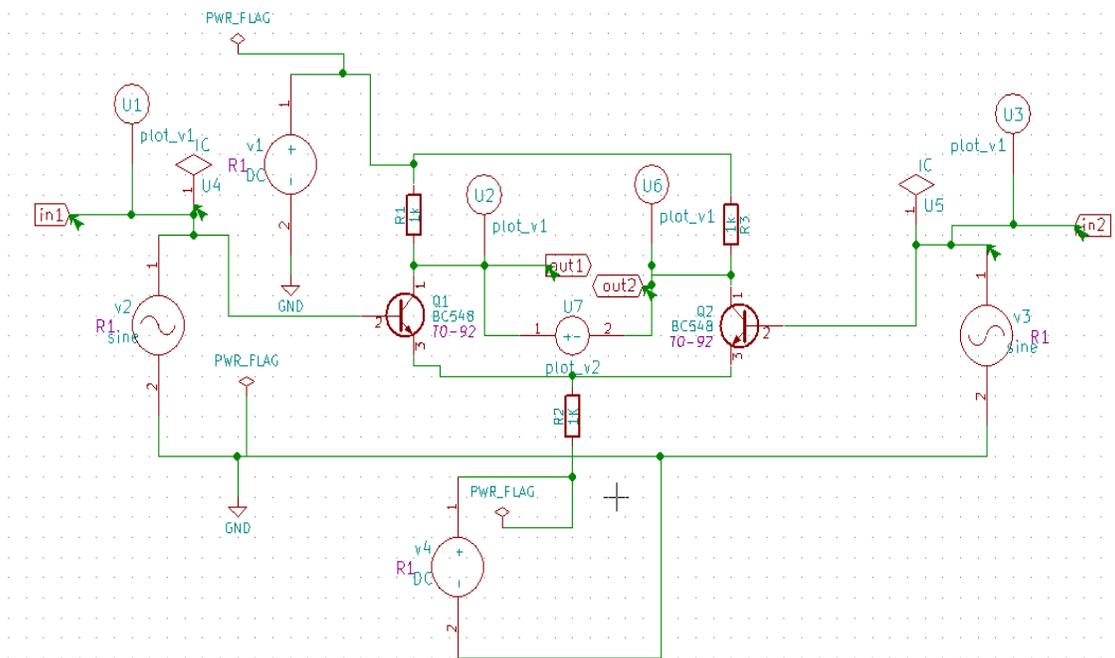


Figure 1: BJT based Differential Amplifier

Simulation Results:

1. Ngspice Plots-

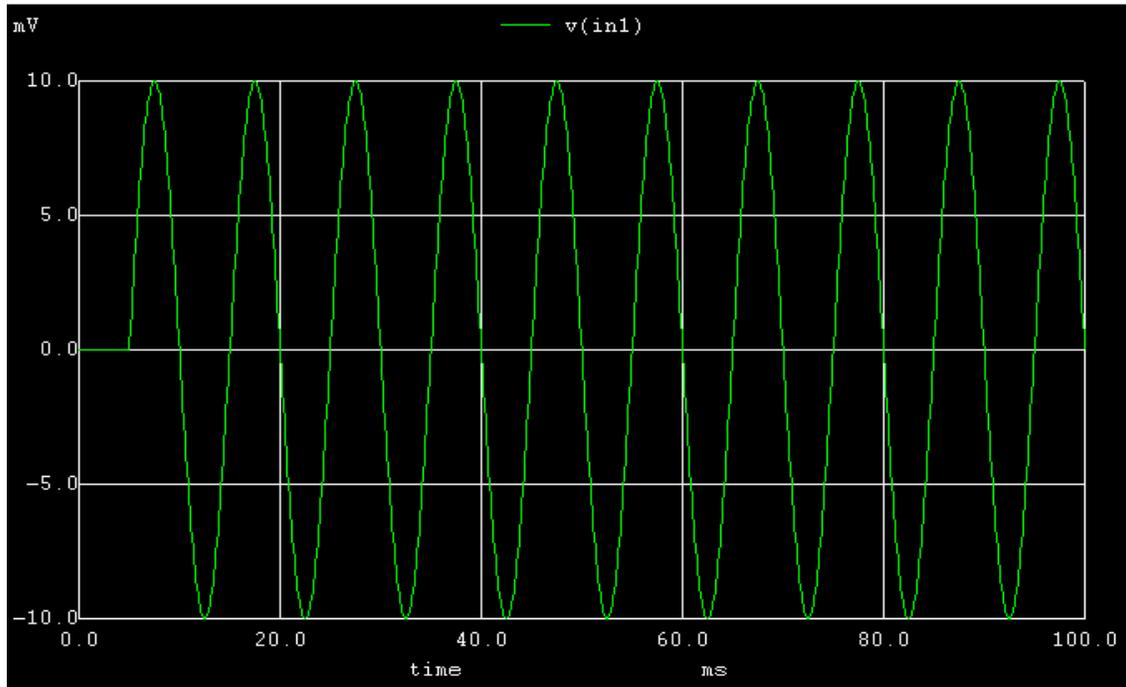


Figure 2: Ngspice Input 1 Plot

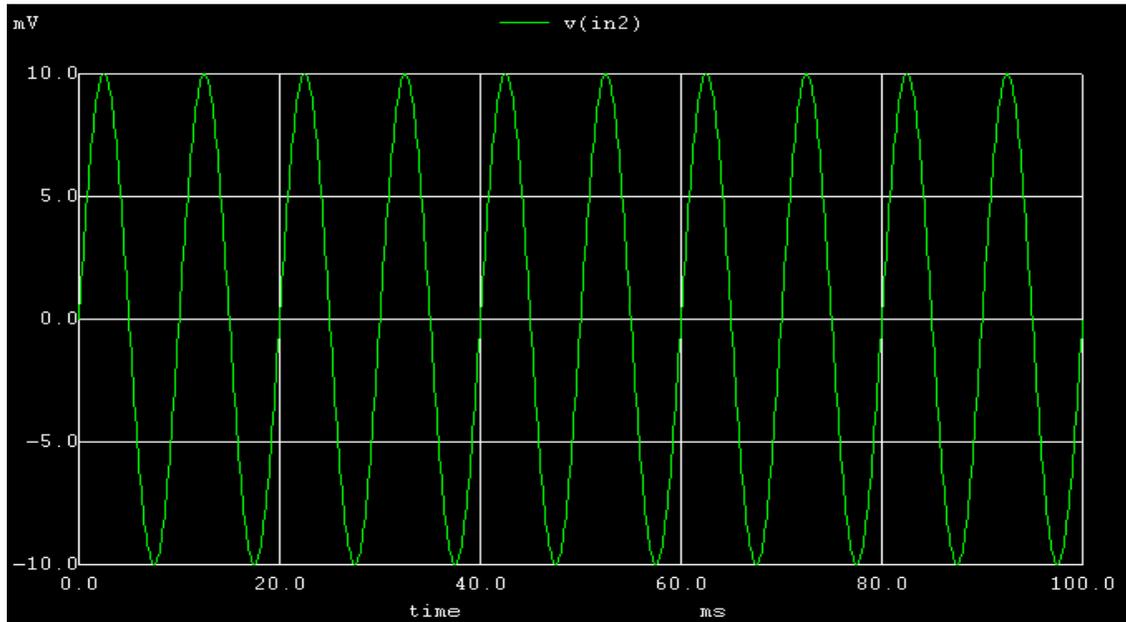


Figure 3: Ngspice Input 2 Plot

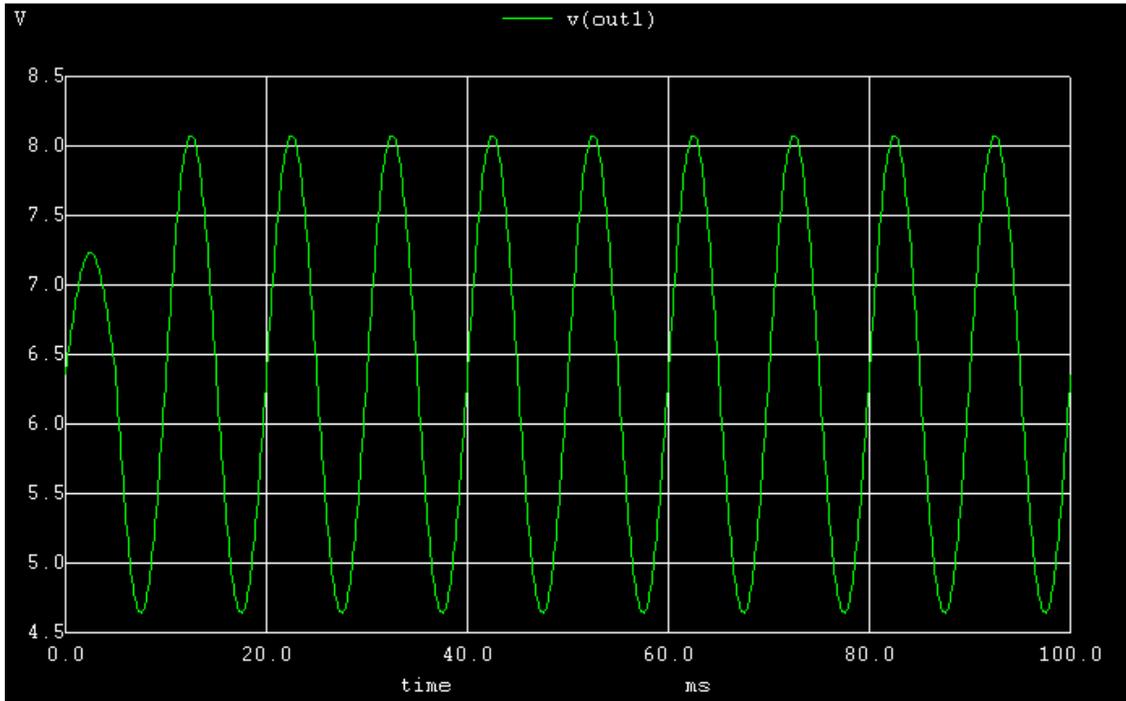


Figure 4: Ngspice Output 1 Plot

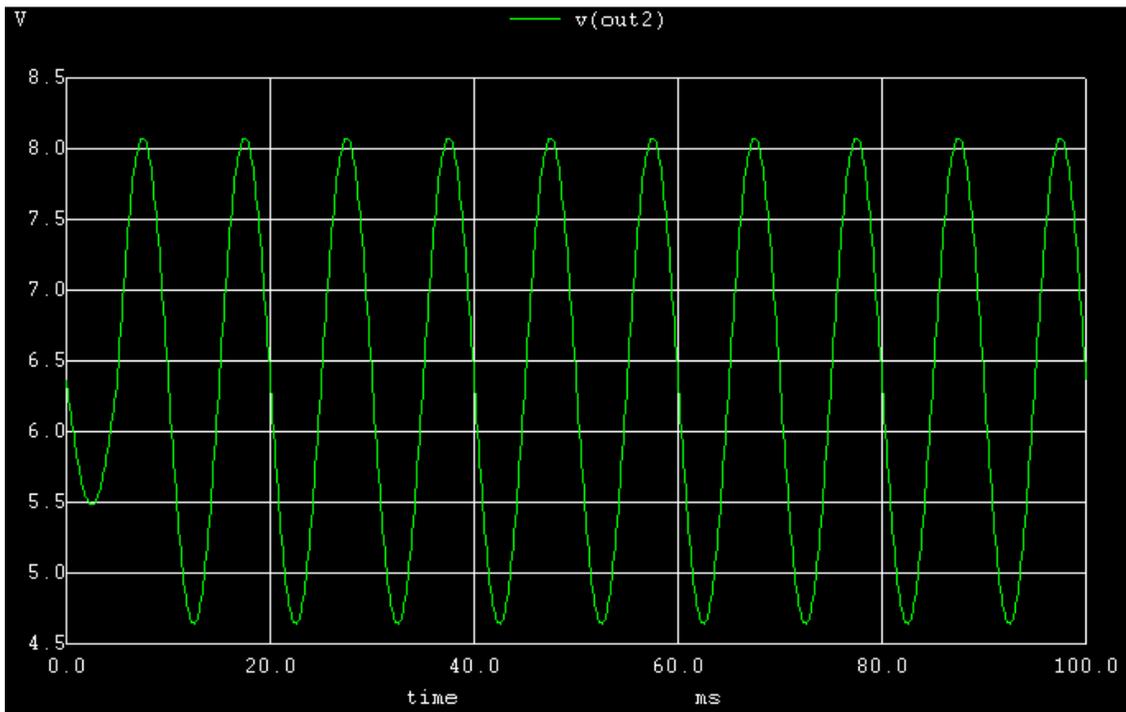


Figure 5: Ngspice Output 2 Plot

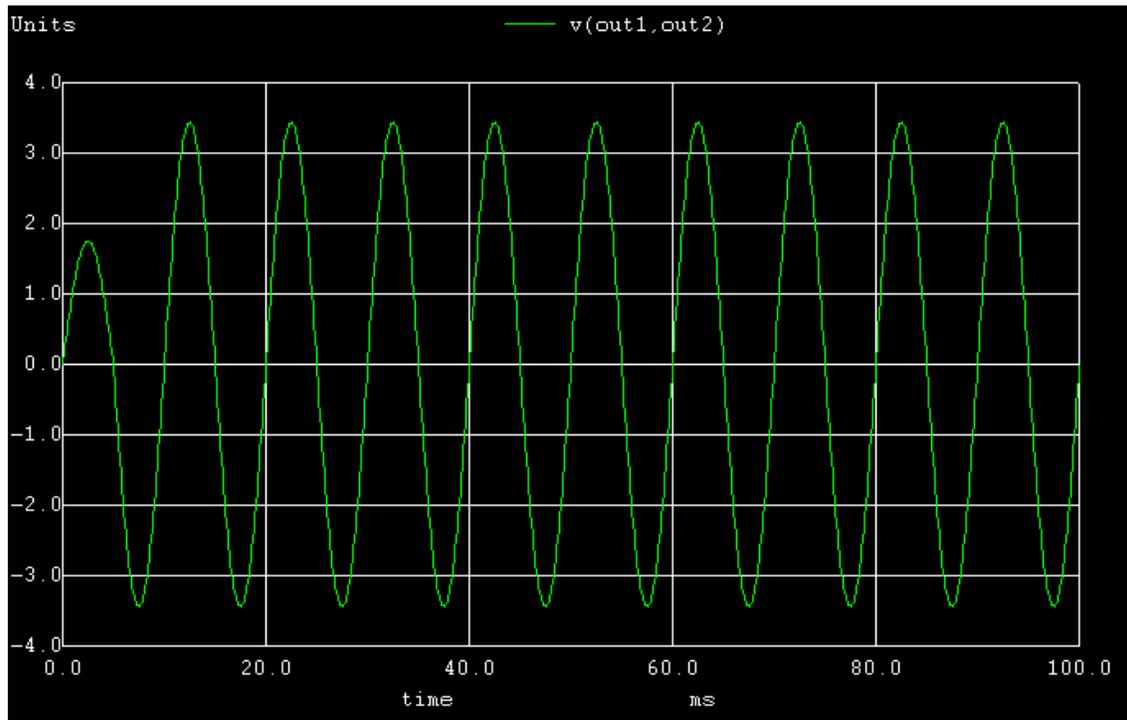


Figure 6: Ngspice Final Output(Output 1, Output2) Plot

2. Python Plots-

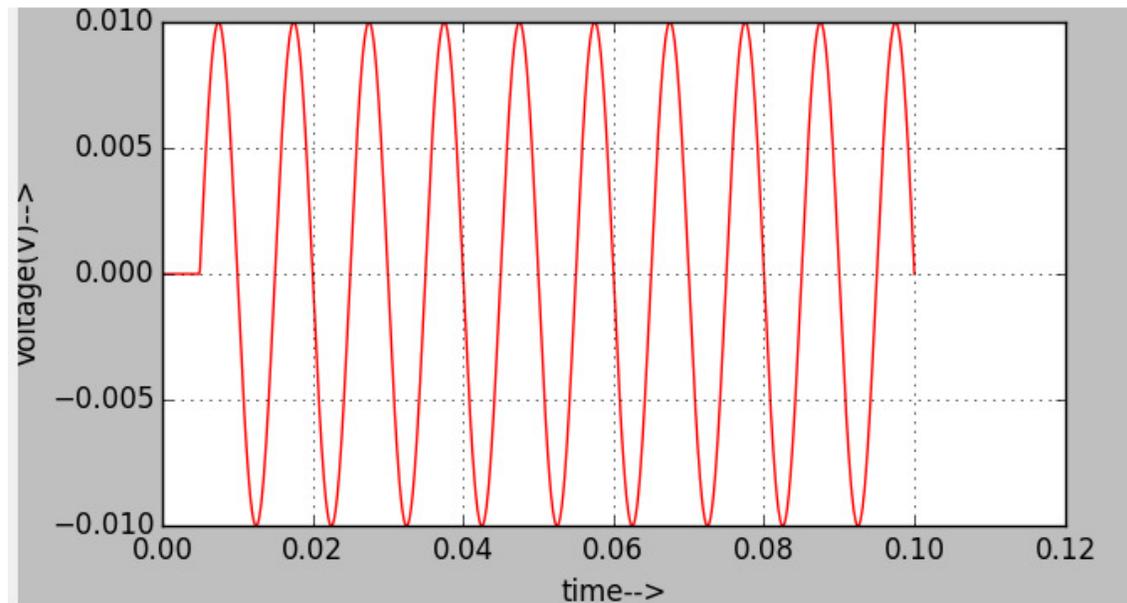


Figure 7: Python Input 1 Plot

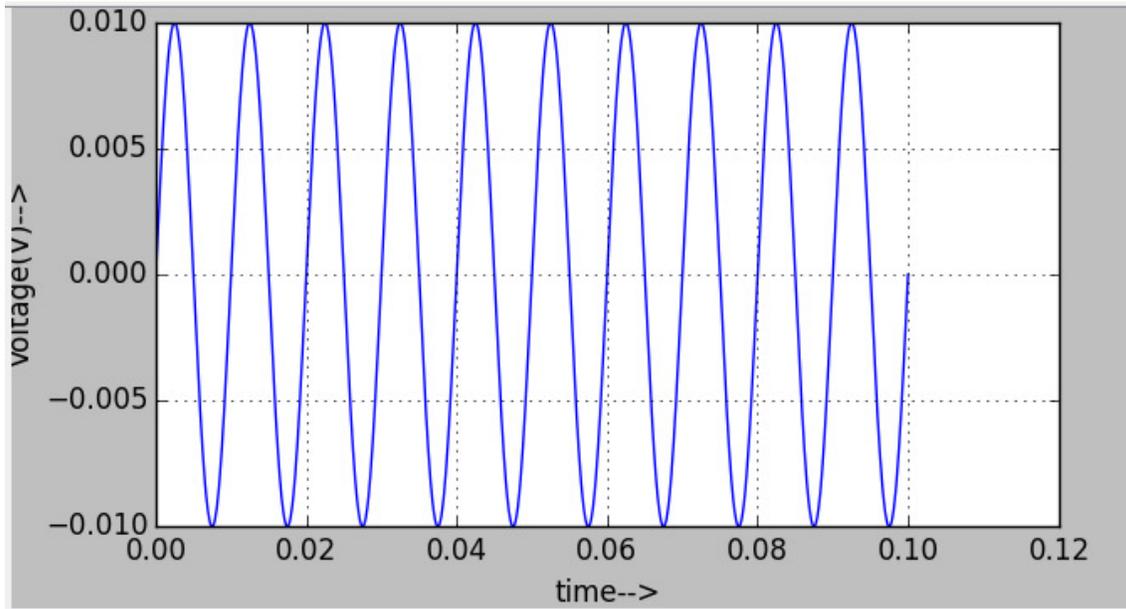


Figure 8: Python Input 2 Plot

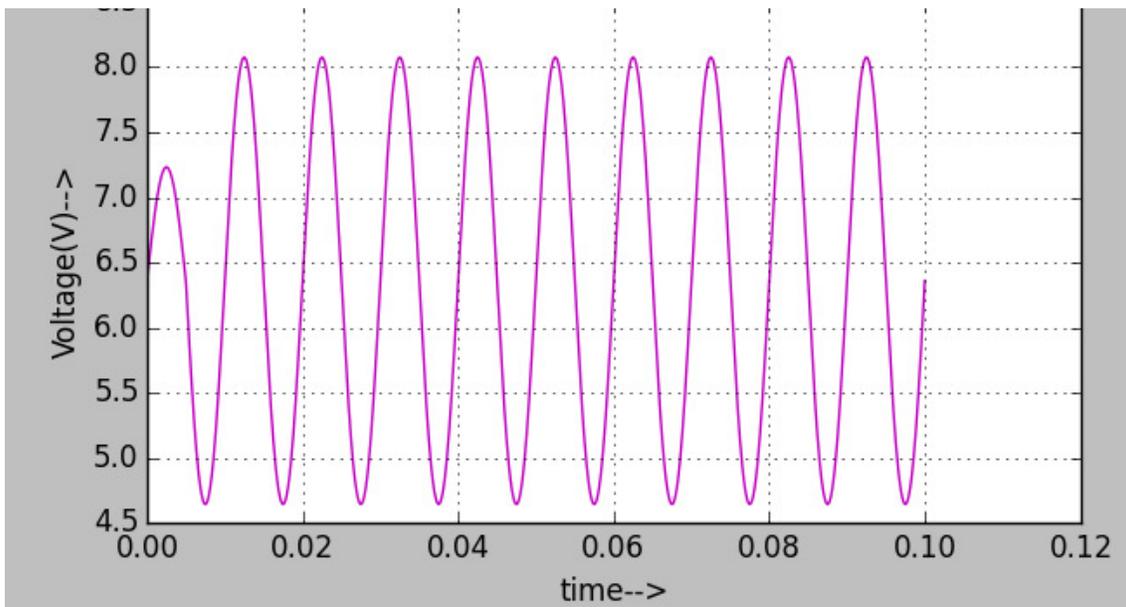


Figure 9: Python Output 1 Plot

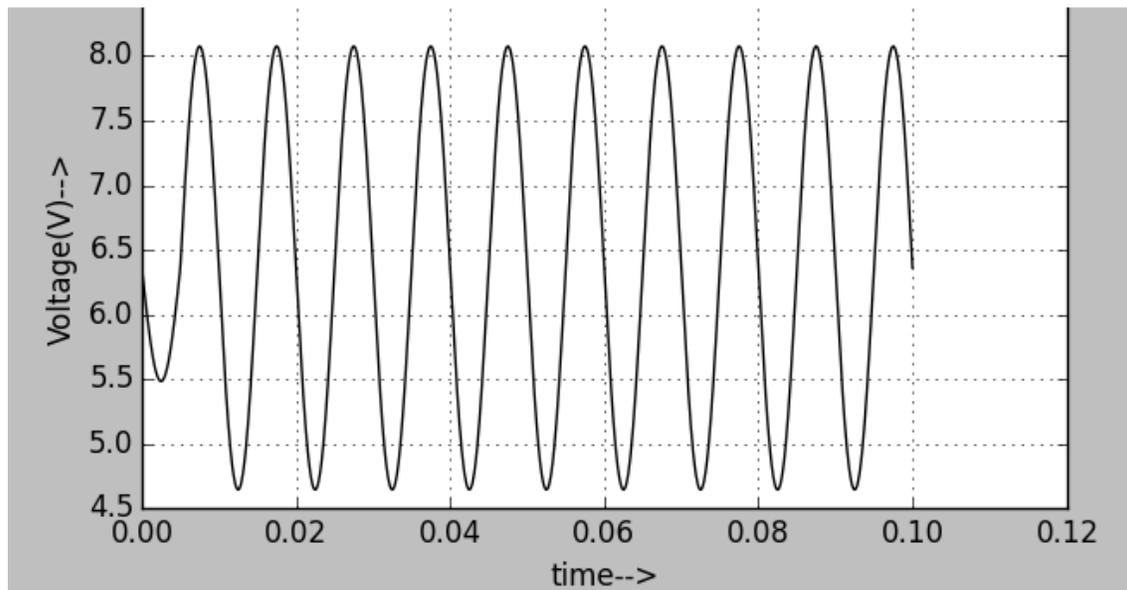


Figure 10: Python Output 2 Plot

Conclusion:

Thus, we have studied the BJT based Differential Amplifier and the simulation plot of ngspice and python plot obtained in eSim.

References:

- 1) <https://www.elprocus.com/differential-amplifier-circuit-working/>
- 2) <http://www.circuitstoday.com/differential-amplifier>
- 3) <https://www.elprocus.com/differential-amplifier-circuit-working/>