



## Title :4 BIT SYNCHRONOUS DOWN-COUNTER


### Abstract :

A counter is a device which stores (and sometimes displays) the number of times a particular event or process has occurred, often in relationship to a clock signal. Counters are used in digital electronics for counting purpose, they can count specific event happening in the circuit. In DOWN COUNTER a counter decreases count for every rising edge of clock.

A 4-bit Synchronous down counter starts its counting sequence from 1111 in binary i.e 15 in decimal and decrement in downward counting sequence by "one" for each clock pulse until it count reaches to 0000 in binary i.e 0 in decimal and then restart new counting cycle by getting reset itself from 1111 again.

**In Synchronous DOWN COUNTER**, the external clock signal is connected to the clock input of EVERY individual flip-flop within the counter so that all of the flip-flops are clocked together simultaneously (in parallel) at the same time giving a fixed time relationship. In other words, changes in the output occur in "synchronization" with the clock signal.


### Circuit Diagram:

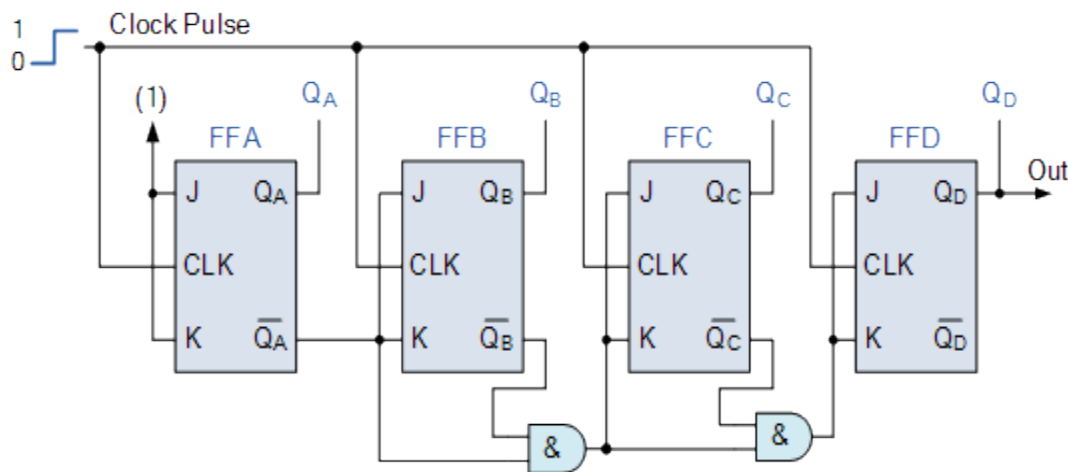


**ESIM Required Components:**

| Synchronous up counter |                   |
|------------------------|-------------------|
| Component Name         | Type              |
| d_and                  | And gate          |
| d_jkff                 | J-K Flip Flop     |
| DC                     | DC voltage source |
| clock                  | clock input       |


**ESIM Circuit design snapshot:**

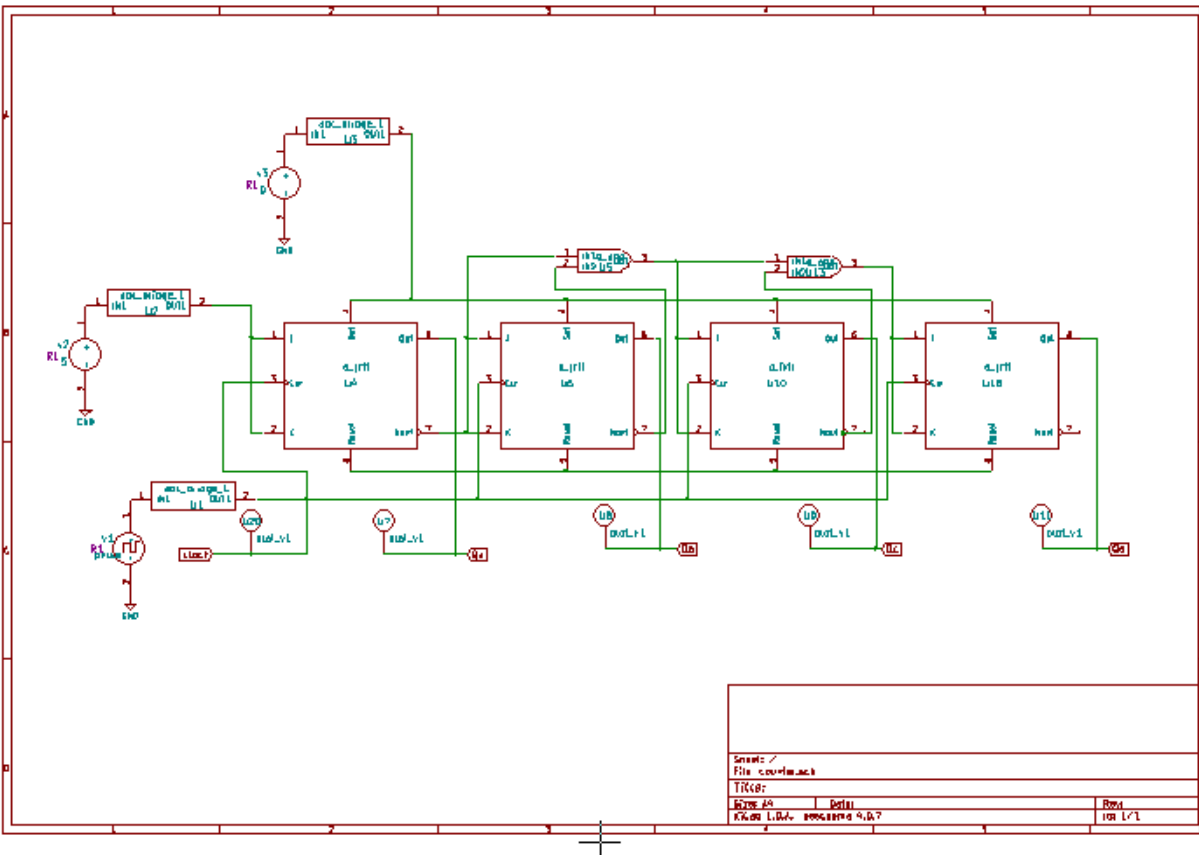


|                   |                 |      |     |
|-------------------|-----------------|------|-----|
| Schematic /       |                 |      |     |
| File counter.mach |                 |      |     |
| Title:            |                 |      |     |
| Layer #0          | Detail          | Rev: |     |
| File: L:\B+       | 2008/08/04 9:07 | rev: | 1/1 |

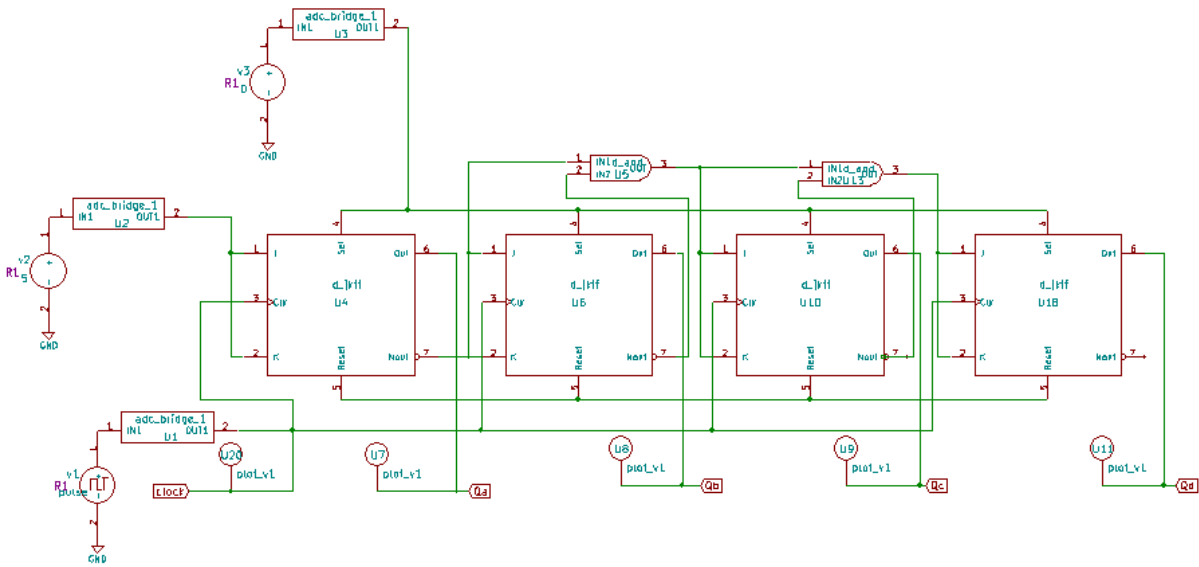


Graph for v(qa) vs time

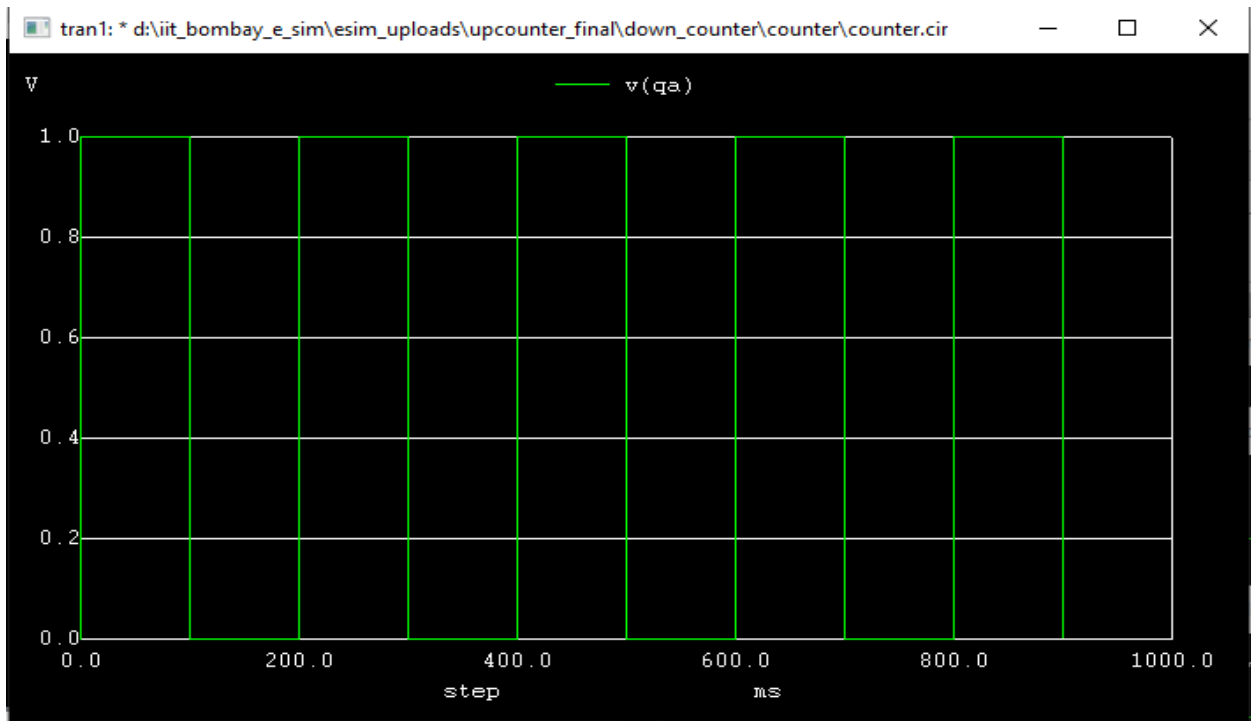


### Graph for $v(qb)$ vs time

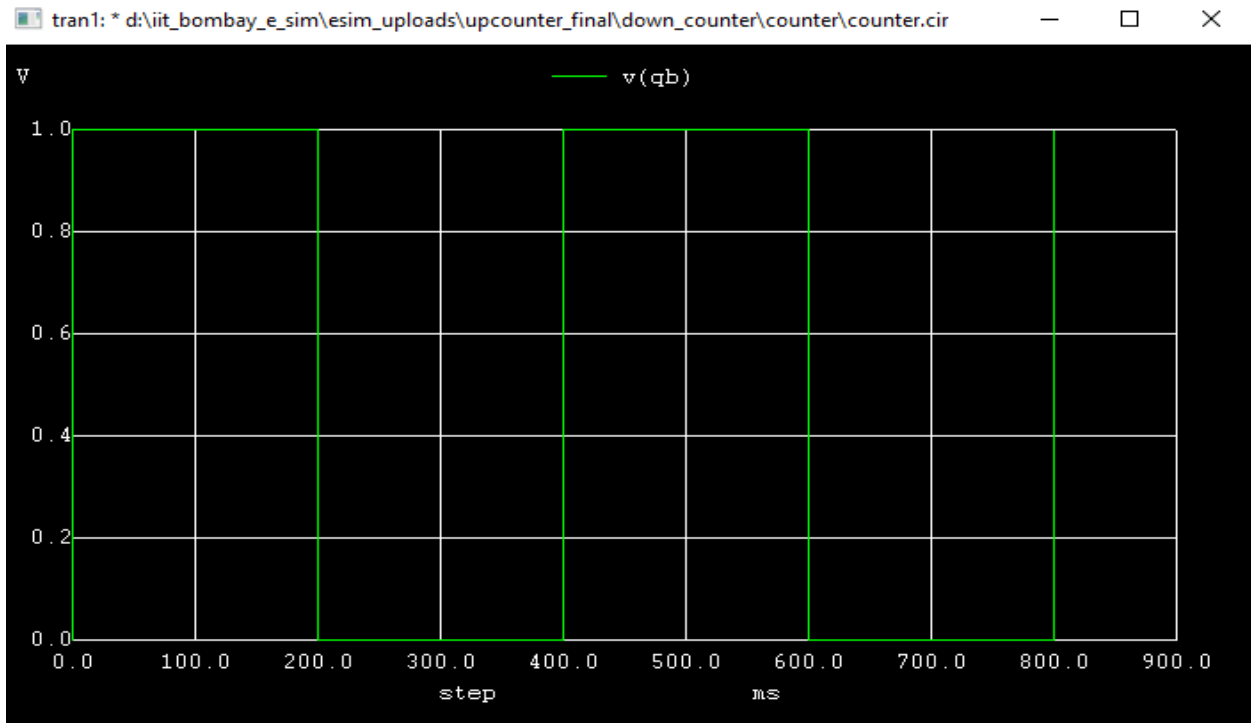

### Graph for $v(qc)$ vs time

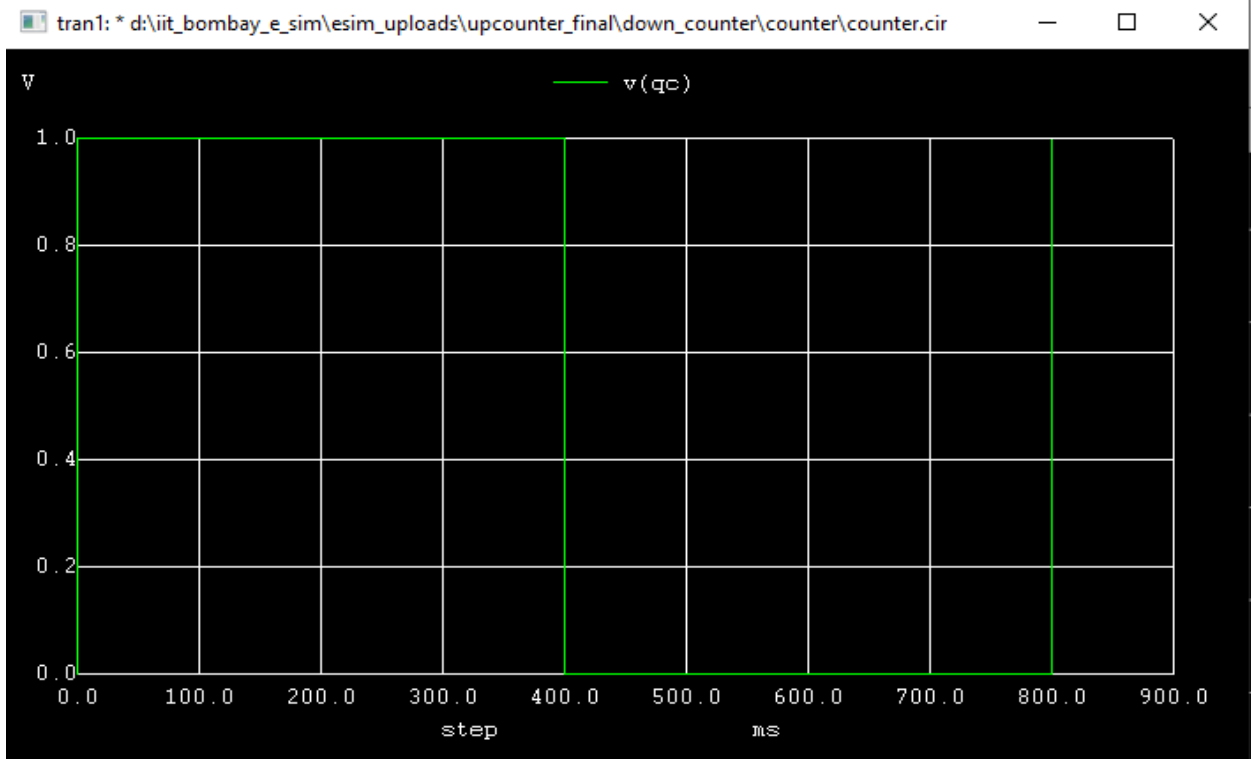

## Graph for v-clock pulse

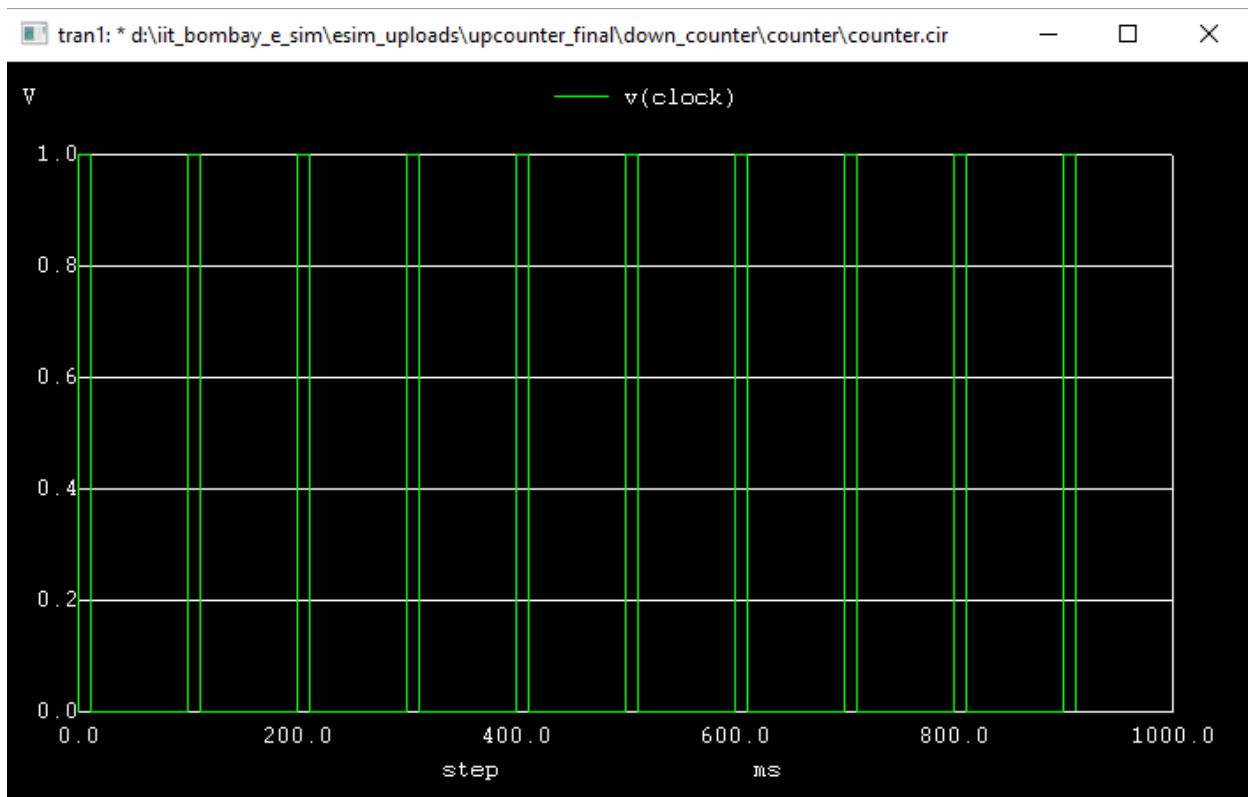

## References:

- [https://www.electronics-tutorials.ws/counter/count\\_3.html](https://www.electronics-tutorials.ws/counter/count_3.html)
- <http://ngspice.sourceforge.net/>